

Question paper

Paper-I

Q-1 A) Select correct alternative and rewrite the sentence. (4)


- 1) To get Thevenin voltage ,you have to -----
 - i) Short the load resistor
 - ii) open the load resistor
 - iii) Short the voltage source
 - iv) open the voltage source
- 2) An ideal current source is one whose internal resistance is -----
 - i) Very High
 - ii) Infinite
 - iii) zero
 - iv) Low
- 3) In ----- meter an internal battery must be used.
 - i) Ohm meter
 - ii) Voltmeter
 - iii) Ammeter
 - iv) Cali meter
- 4) In purely ----- circuit, the current leads the voltage by 90° .
 - i) Resistive
 - ii) Capacitive
 - iii) Inductive
 - iv) Active

Q-1) B) Answer any two of the following questions. (6)

- 1) State Thevenin's theorem .Which steps should be followed while using this theorem?
- 2) Define for AC :i) Peak Value ii) Average value iii) RMS value
- 3) Explain construction Ammeter using PMMC mechanism with diagram.

Q-2) A) Answer any two of the following questions. (6)

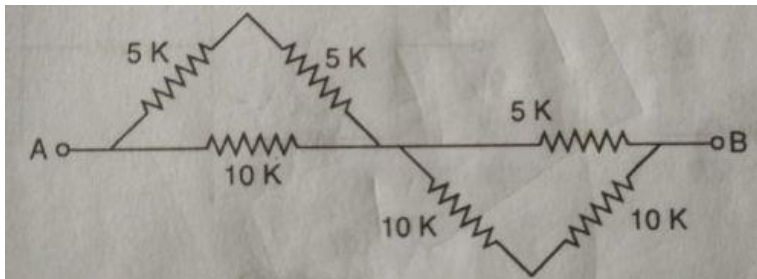
- 1) Find the total resistance across AB.



- 2) Compare AC voltage and DC voltage.
- 3) Write a note on multimeter.


Q.2) B) Answer any one of the following question. (4)

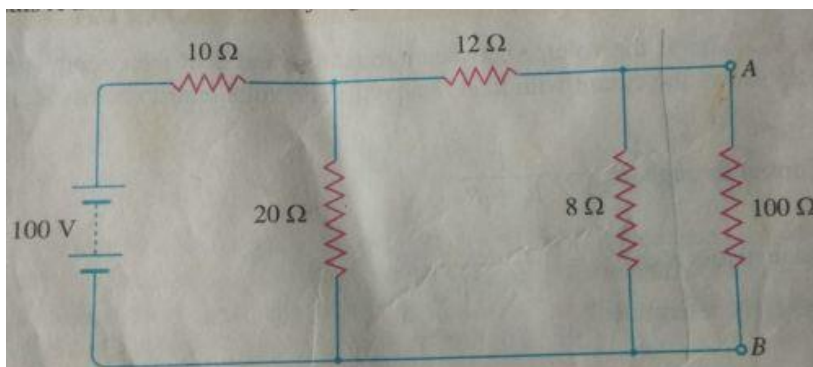- 1) Using Thevenin's theorem, find the current through 100Ω resistance Connected across terminals A and B in following circuit.



- 2) Using Norton's theorem, find the current through 8Ω resistor in network

shown in fig. below

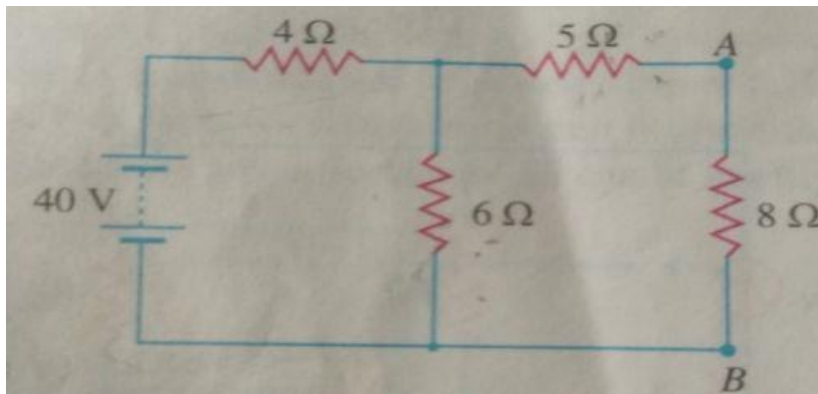

Q-3) A) Answer any two of the following questions. (6)

- 1) State superposition theorem for which type of components this theorem can be applied?
- 2) Explain the terms; importance, inductive reactance and Capacitive reactance.
- 3) Explain the conversion of galvanometer into DC voltmeter.

Q-3) B) Answer any one of the following. (4)


- 1) Find the voltmeter reading and error in measurement of Voltage in the following circuit. Voltmeter has sensitivity of $2\text{k}\Omega/\text{V}$ is used at a range of 0 – 50 volts.
- 2) The resonant frequency of LC circuit is 1KHz. Calculate the value of inductance, if the capacitance is $50\mu\text{F}$.

Q-4) A) Answer any two of the following questions. (6)

- 1) State Kirchoff's law with suitable examples.
- 2) Explain the importance of time factor in frequency and phase.
- 3) What are the precautions that must be observed by using ammeter.

Q-4) B) Answer any one of the following. (4)

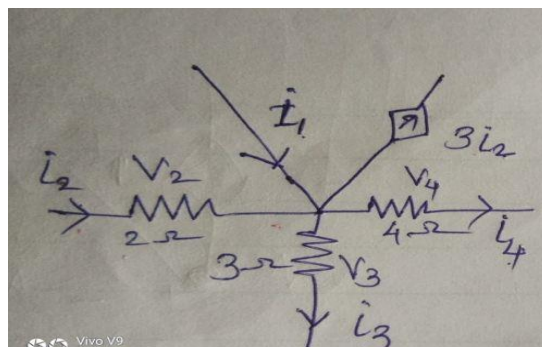- 1) A PMMC meter carries maximum current 15 mA when a Potential difference of 75 V is applied across it . How will you convert it into voltmeter for measuring 150Volts?
- 2) Calculate currents. i_2, i_3, i_4 .
Given $i_1 = 4\text{A}, V_3 = 3\text{V}$




Q-5) A) Answer any two of the following. (6)

- 1) State KCL and explain its sign conventions
- 2) Explain the generation of alternating voltage using rotary generator.
- 3) What are the precautions observed while using voltmeter.

Q-5) B) Answer any one of the following. (4)

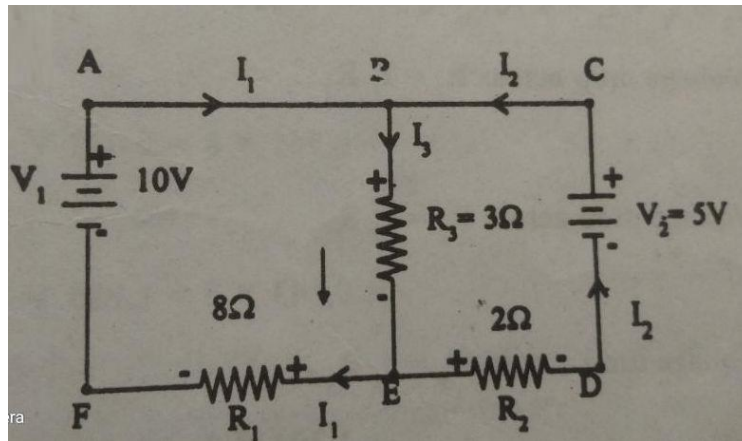- 1) A galvanometer has a sensitivity of $20 \text{ k}\Omega/\text{V}$. find the resistance required to use it as a voltmeter of range 100 V . the resistance of galvanometer is 200Ω .
- 2) Using Kirchhoff's laws, calculate current through each resistor and voltage drop across each resistor for the circuit shown below.



OR

Q-5) A) Answer any two of the following. (6)

- 1) State and explain Maximum power transfer theorem.
- 2) State and explain any two types of AC sources.
- 3) Define voltmeter sensitivity. Write equation using sensitivity for the multiplier resistor.

Q-5) B) Answer any one of the following. (4)

- 1) Design a multirange voltmeter using galvanometer of full scale deflection of $500\mu\text{A}$ and resistance 100Ω with ranges of 10V and 50V . draw circuit diagram.
- 2) Pic – to – pic voltage of sinewave is 350V . calculate the average value and rms value of the voltage.