

NRT/KS/19/2027

Bachelor of Science (B.Sc.) Semester—I Examination
ELECTRONICS (Fundamentals of Digital Electronics)
Optional Paper—2

Time : Three Hours]

[Maximum Marks : 50

N.B. :— (1) **ALL** questions are compulsory and carry equal marks.

(2) Draw neat and well labelled diagrams wherever necessary.

EITHER

1. (A) Do as directed :

(i) $(1010)_2 = ()_8$

(ii) $(60)_{10} = ()_{16}$

(iii) $(1234)_{10} = ()_{BCD}$.

Explain how negative integers are represented using 2's complement number representation.

Explain BCD and gray code.

3+4+3

OR

(B) Explain the difference between weighted and non-weighted code. Give two examples of each. Explain any one weighted and non-weighted code in detail. Give their limitation and advantages. Why Excess-3 code is called as self complementary code ?

2+6+2

EITHER

2. (A) Draw the symbol and truth table of XOR gate using basic logic gates. Explain why NOR and NAND gates are called universal building blocks.

3+7

OR

(B) State and prove DeMorgan's theorems. Draw their logic diagrams. Simplify the following equation using Boolean laws :

(i) $Y = ABC + \overline{BCD} + \overline{ABC}$

(ii) Prove : $\overline{AB} + \overline{AC} + \overline{BC} = \overline{AC} + \overline{BC}$

(iii) Prove : $A + \overline{AB} = A + B$.

4+6

EITHER

3. (A) Explain what are standard SOP and POS form of Boolean equation with examples. Design binary to gray code converting using K-map.

4+6

OR(B) Define Quad, pair and octet. Simplify using K-maps $F(ABCD) = \sum m(0, 3, 5, 6, 9, 10, 12, 15)$. Plot K-map and write simplified equation.

3+7

EITHER

4. (A) With logic diagram and truth table. Explain the working of :

(i) Full Adder

(ii) Full Subtractor.

5+5

OR

(B) Draw the logic diagram and explain the working of 4 : 1 multiplexer using logic gates. Draw the circuit diagram and explain the working of even parity generator.

5+5

5. Solve any *ten* :

(A) Write gray code for decimal 9.

(B) Why binary number system is used in the working of computer ?

(C) Write the 2's complement of $(1010)_2$.

(D) Draw the pin diagram of IC 7400.

(E) State the Duality theorem.

(F) Using truth table prove the relation $A \oplus B = \overline{A} \oplus \overline{B}$.

(G) How many variables are eliminated in a octet of K map ?

(H) Give the truth table of XNOR gate.

(I) What is POS ?

(J) What is encoder ?

(K) Define odd parity generator.

(L) Write the limitation of half adder.

1×10