

NKT/KS/17/5059

Bachelor of Science (B.Sc.) Semester—I (C.B.S.) Examination

ELECTRONICS

(Electronic Components, Network Theorems)

Compulsory Paper—1

Time : Three Hours]

[Maximum Marks : 50

N.B. :— (1) **ALL** questions are compulsory and carry equal marks.

(2) Draw neat and well labelled diagram wherever necessary.

EITHER


1. (A) Explain 4 band colour coding methods used in carbon resistor. Find the value of resistance with colour code sequence Brown, Black, Orange, Gold. Find the colour code sequence for $47K \pm 10\%$ resistance. 6+2+2

OR

- (B) Draw the block diagram of CRO and explain the function of each block in brief. 10

EITHER

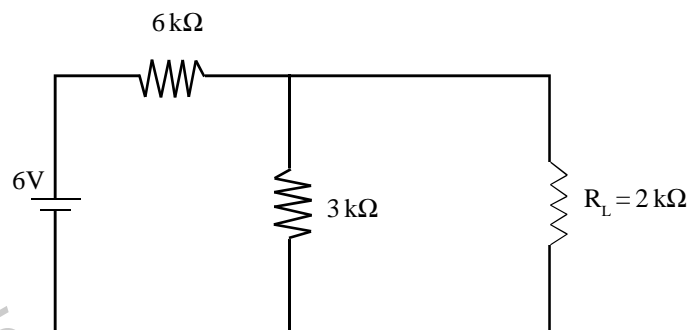
2. (A) State Norton's theorem and explain the method of calculating I_N and R_N for a Norton equivalent circuit with suitable example. Calculate the current through $R_L = 2K\Omega$ resistor using Thevenin theorem given below :



5+5

OR

- (B) State and explain Kirchoff's current and voltage law. Using superposition theorem calculate the current flowing through $6K\Omega$ resistor in the circuit : 5+5

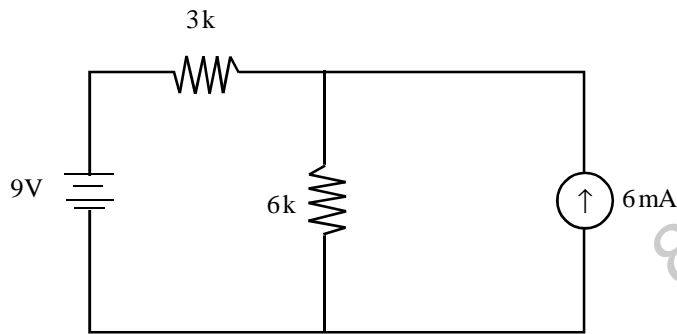**EITHER**

3. (A) What are intrinsic and extrinsic semiconductors ? Explain formation of P-type and N-type semiconductor. Draw and explain energy band diagram for each. 3+3+4

OR

- (B) Explain avalanche effect and zener effect. What is LED ? Explain how charge carrier recombination produces light. Which segments need to be activated to display the number '3' in seven segment display ? 5+3+2

EITHER

4. (A) What is Transistor ? Explain construction of NPN transistor and describe in detail the transistor action. Draw the circuit diagram and explain input and output characteristics of transistor in CE mode. 5+5

OR

- (B) Explain using neat circuit diagram the operation of a transistor as a switch. Explain the voltage divider method for biasing of transistor. State their advantages and disadvantages. 5+5

5. Solve any **ten** :

- (a) What is reactance of capacitor C ?
 (b) State applications of Relay.

- (c) Define Switch.
- (d) State Ohm's law.
- (e) State Superposition theorem.
- (f) State KVL.
- (g) What is Cut-in voltage of Germanium diode ?
- (h) What is conduction band ?
- (i) Draw the symbol of zener diode.
- (j) Draw the symbol of npn transistor.
- (k) What is biasing in transistor ?
- (l) What is operating point in o/p characteristics of transistor ?

1×10