

Bachelor of Science (B.Sc.) Semester—I Examination

ELECTRONICS : ELECTRONICS COMPONENTS AND NETWORK ANALYSIS

Optional Paper—I

Time : Three Hours]

[Maximum Marks : 50

- Note :—(1) All questions are compulsory.
 (2) All questions carry equal marks.
 (3) Draw neat diagrams wherever necessary.

EITHER


1. (A) What is resistor ? Draw the symbol of resistor. State different types of resistors. List the different functions of resistor. Explain the series and parallel combination of resistor with a suitable diagrams. 1+1+2+2+4=10

OR

- (B) What is inductor ? State different types of inductors. List the factors affecting the inductance of an inductor. Explain the construction and working of transformer in brief. 1+1+2+6=10

EITHER

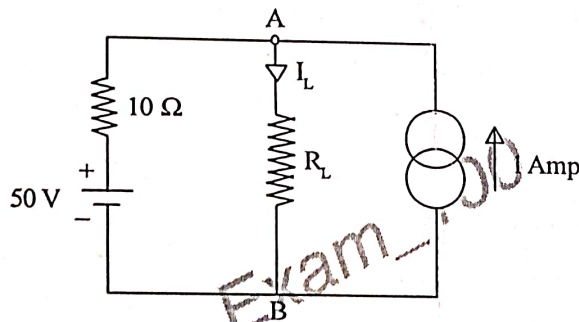2. (A) State and prove Maximum Power Transfer Theorem. Find the value of load resistance, R_L which will absorb maximum power and determine the maximum power in the network shown :



5+5=10

OR

- (B) (i) State and explain Norton's Theorem.
 (ii) State and explain Thevenin's Theorem. Write the steps to convert Thevenin's equivalent circuit into Norton's equivalent circuit with suitable diagram. 4+6=10

EITHER

3. (A) What is sinusoidal waveform ? Explain the generation of alternating voltage using rotary generator. Define the following terms for AC. 1+4+3+2=10
- (i) Peak Value
 - (ii) Average Value
 - (iii) RMS Value
- Explain the concept of phase angle with phasor diagram.

OR

- (B) What is impedance ? Explain capacitive and inductive reactance. 1+2+2=5
- (C) Define Resonance. Explain Parallel Resonance Circuit with Parallel Resonance Curve. 1+4=5

EITHER

4. (A) Describe the construction and working of a Linear Variable Differential Transducer (LVDT) in detail. List the advantages and disadvantages of LVDT. 8+2=10

OR

- (B) What is Piezoelectric effect ? Explain the process of generation of electrical charges in piezoelectric crystal. Draw the diagram of piezoelectric transducer and explain its working in brief. 2+4+4=10

5. Solve any TEN :

- (a) Draw the symbol of SPDT switch.
- (b) What is relay ?
- (c) What is Capacitor ? Draw the symbol of variable capacitor.
- (d) Draw the circuit symbol of ideal and practical voltage source.
- (e) State Superposition Theorem.
- (f) State KCL.
- (g) Write the unit of frequency of sine wave.
- (h) Define RMS Value of sine wave.
- (i) What is bandwidth ?
- (j) What do you understand by the term PTC with respect to thermistor ?
- (k) What is active transducer ?
- (l) What is Thermocouple ?

1×10=10